

General Instructions

- The assignments will help you learn Verilog as a Hardware Description Language and how hardware circuits can be developed using Verilog and FPGA.
- You have to come to the lab during your lab session to carry out the experiments using the FPGA board. You are expected to write the Verilog modules before coming to the lab. Your TAs will check your results and grade your work during the lab session.
- You have to submit the code artifacts through CANVAS.
- Only one member of each group has to submit the assignment. Please Make sure that there is no duplicate submission from your group.
- The maximum possible deadline extension is 2 days. For the extension for one day after the deadline, there will be a penalty of 10% of the grade. For the second day extension, the penalty is another 20% of the grade. No assignment submission will be accepted after 48 hours of the deadline.
- Sharing of the solution outside the group is strictly prohibited. If found guilty, both the involved groups will get 0 in the assignment.
- Each group member should equally contribute to every assignment and should fully understand the submitted solution. The TAs may ask any group member to explain the solution.

Resources

- **Xilinx Spartan 3E FPGA Starter Board**

You will use Xilinx Spartan 3E FPGA Starter Board for your Verilog Assignments.

Here is the manual for the FPGA Kit:

https://www.xilinx.com/support/documentation/boards_and_kits/ug230.pdf

- **Xilinx ISE WebPACK Design Software**

You can use Xilinx ISE WebPACK Design Software for writing and simulating your Verilog programs.

The software can be downloaded from the following location:

<https://www.xilinx.com/support/download/index.html/content/xilinx/en/downloadNav/design-tools.html>

Here are some resources to install the software:

<https://embeddedmicro.com/tutorials/mojo-software-and-updates/installing-ise>

<http://dreamrunner.org/blog/2012/09/12/install-xilinx-ise-on-the-ubuntu/>

- **Verilog Textbook**

Pong P. Chu. FPGA Prototyping by Verilog Examples: Xilinx Spartan-3 Version, John Wiley & Sons, Inc., 2008.

<http://www2.dc.ufscar.br/~marcondes/netfpga/FPGAPrototypingByVerilogExamples.pdf>

Assignment 1 (10 points)

Lab Session: (during the week of March 06, 2017 - March 10, 2017)

Deadline for submission: 11:59 pm on March 10, 2017

Objectives:

- To learn how to use Xilinx ISE WebPACK design software to develop a Verilog module for a hardware circuit, simulate and test it, and program the FPGA chip to implement the hardware.
- To get familiar with the input-output mechanisms of the Xilinx Spartan 3E FPGA kit: slide switches, push-button switches, LEDs and LCD Screen.

Problems:**1. Blinking a LED** (2 points)

Follow the instructions in the following tutorial to blink a LED in your FPGA Board.

<https://therobotfix.wordpress.com/2011/06/27/getting-started-with-spartan-3e-fpga-and-verilog/>

This tutorial illustrates how to use the ISE Webpack design software and describes all the steps to develop a hardware circuit using FPGA.

References:

- (1) Xilinx Spartan 3E FPGA board Manual (Chapter 2, Chapter 3)

2. Printing in the LCD display (3 points)

Write a Verilog module and a constraint file to display “Computer Organization” in the LCD screen of your FPGA Fit. The LCD display has two rows. The word “Computer” should be displayed in the first row and the word “Organization” should be displayed in the second row.

References:

- (1) The following Quora post discusses how to display “Hello World” on the LCD display of the Spartan 3E FPGA board:

<https://www.quora.com/What-is-the-Verilog-code-to-display-a-character-on-an-LCD-screen-of-the-Spartan-3E-XC3S400-FPGA-kit>

- (2) Xilinx Spartan 3E FPGA board Manual (Chapter 5)

3a. Comparing two 2-bits binary number (2 points)

(a) Write a Verilog module *eq1* to compare two bits. The output should be 1 if the two bits are equal. Write a Verilog module *eq2* to compare two 2-bit binary numbers. The program should return 1 if the two numbers are equal. Use the module *eq1* to implement the module *eq2*.

(b) Write a Verilog Test Fixture containing at least four different test cases. Use the ISim simulator to simulate the Verilog module.

(c) Write a constraint file to use the 4 sliding switches to input two 2-bit binary numbers. Use one of the LEDs to indicate the output.

(d) Synthesize and implement your Verilog module to generate a configuration file and download the configuration file to the FPGA chip.

(e) Move the sliding switches to on and off positions to generate different 2-bit binary numbers as input and check the LED output to ensure that your circuit is correct.

References:

- (1) Xilinx Spartan 3E FPGA board Manual (Chapter 2)
- (2) Your Verilog Textbook (Chapter 2)

3b. Comparing two 4-bits binary number (3 points)

(a) Write a Verilog module *eq4* to compare two 4-bit binary numbers. The program should return 1 if the two numbers are equal. Use the module *eq2* to implement the module *eq4*.

(b) Write a Verilog Test Fixture containing at least four different test cases. Use the ISim simulator to simulate the Verilog module.

(c) The Xilinx Spartan 3E FPGA board has only four sliding switches. That allows you to input only one 4-bit binary number. To input more data you use push-button switches. You can position the slide switches and press a push button to enter a binary number. You repeat the process with another push button to enter the second number.

Update the Verilog module to incorporate the input mechanism using slide switches and push-button switches.

Write a constraint file to use 4 sliding switches and two push buttons to input the two 4-bit binary numbers. Use one of the LEDs to indicate the output.

(d) Synthesize and implement your Verilog module to generate a configuration file and download the configuration file to the FPGA kit.

(e) Move the sliding switches to on or off position to generate different 4-bit binary numbers. Use the two push buttons to capture the numbers. Check the LED output to ensure that your circuit is correct.

References:

- (1) Xilinx Spartan 3E FPGA board Manual (Chapter 2)
- (2) Your Verilog Textbook (Chapter 4, Section 4.5.1 for an example of using slide switch and push-button switch together to input multiple binary numbers)